

Brahma Valley College of Technical Education, Anjaneri, Nashik  
Prelim Exam

**Course & Code:** EJ4G  
**Subject:** LIC(17445)

**Date:** 10/03/2014  
**Time:** 9.30 am to 12.30 pm

**Q1.A) Attempt any SIX (12 Marks)**

- a. Define:
  - i) Input offset voltage
  - ii) Slew Rate
- b. Draw circuit diagram of basic differentiator using op-amp
- c. List any four specifications of IC LM 324
- d. State the need of signal conditioning (any two points)
- e. Define sample period and hold period with reference to sample and hold circuit
- f. Define:
  - i) Q factor of filter
  - ii) Passband of filter
- g. Draw circuit diagram of narrow band reject filter using op-amp
- h. State functions of following pins of IC 555
  - i) Threshold
  - ii) Discharge

**Q1.B) Attempt any TWO (08 Marks)**

- a. Describe the function of input stage and level shifting stage of op-amp with its block diagram
- b. State ideal values of following parameters of op-amp as well as state typical values of following parameters of op-amp IC 741
- c. Describe the term dual i/p balanced o/p differential amplifier and dual i/p unbalanced o/p differential amplifier and draw single i/p unbalanced o/p differential amplifier

**Q2. Attempt any FOUR (16 Marks)**


- a. Compare open loop and closed loop configuration of op-amp on following basis
  - a. Circuit Diagram
  - b. Gain
  - c. Bandwidth
  - d. Application
- b. Describe virtual ground and virtual short concept with reference to op-amp.
- c. Draw closed loop Non-Inverting amplifier using op-amp and derive expression for its gain.
- d. Derive the expression for relation between i/p and o/p of basic integrator and draw basic integrator.
- e. Design and draw the circuit for the following operation using op-amp
- f.  $V_o = 2V_1 + V_2 - 5V_3$
- g. Suggest op-amp based circuit to convert square wave to triangular wave and draw the circuit diagram with input and output waveform.

**Q3. Attempt any FOUR (16 Marks)**


- a. Describe the operation of instrumentation amplifier with transducer bridge with help of neat circuit diagram.
- b. Draw circuit diagram of grounded load type V-I converter and derive expression for its output.
- c. State the needs of peak to peak detector and draw its circuit diagram.
- d. Draw and describe following op-amp based operation using log and antilog amplifier  $V_o = V_1 \times V_2$
- e. Draw circuit diagram and input output waveforms of inverting ZCD and non-inverting ZCD
- f. Describe the operation of op-amp based Schmitt trigger for sine to square wave conversion with the help of its circuit diagram

**Q4. Attempt any FOUR (16 Marks)**

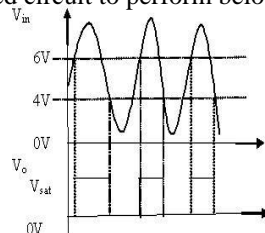- a. Suggest an OPAMP based circuit to perform below operation



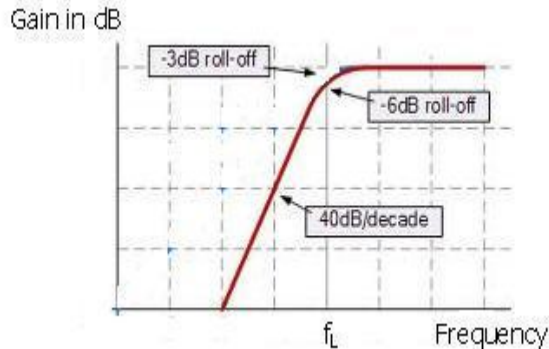- b. Design and draw low pass filter with cut off frequency 2 KHz and passband gain of 2.  
 c. Suggest and draw op-amp based circuit using Butterworth filter to fulfill following response



- d. Describe the operation of wide bandpass filter with the help of circuit diagram  
 e. Draw the circuit diagram of op-amp based filter circuit which provides following response and describe its operation.  
 f. Classify the op-amp filters on following basis:  
 1. Components used  
 2. Frequency range  
 3. Frequency response  
 4. Nature of passband and stopband

**Q5. Attempt any FOUR**

**(16 Marks)**

- Draw the block diagram of SE 555. State the function of both internal transistors in IC 555.
- Draw and describe the operation of water level controller using IC 555.
- Draw and describe the operation of frequency divider using IC 555.
- Describe the operation of phase detector and role of VCO in PLL.
- Define and state the expression for lock range and capture range of PLL.
- Describe with the help of block diagram the operation of FM demodulator using PLL.

**Q6. Attempt any FOUR**

**(16 Marks)**

- Draw the block diagram of VCO using IC 555. Describe how output frequency varies with the variation in voltage applied to pin 5 of IC 555.
- Draw the circuit diagram of square wave generator using IC 555. State the purpose of external diode used in the circuit and state expression of its output frequency.
- Design and draw monostable multivibrator using IC 555 with  $T_p = 1\text{ms}$ .
- Design and draw op-amp based Wein Bridge oscillator for frequency 1KHz.
- Draw and describe operation of Bistable multivibrator using op-amp.
- How much is overall phase shift in op-amp based phase shift oscillator and how it is achieved. Draw its circuit diagram.